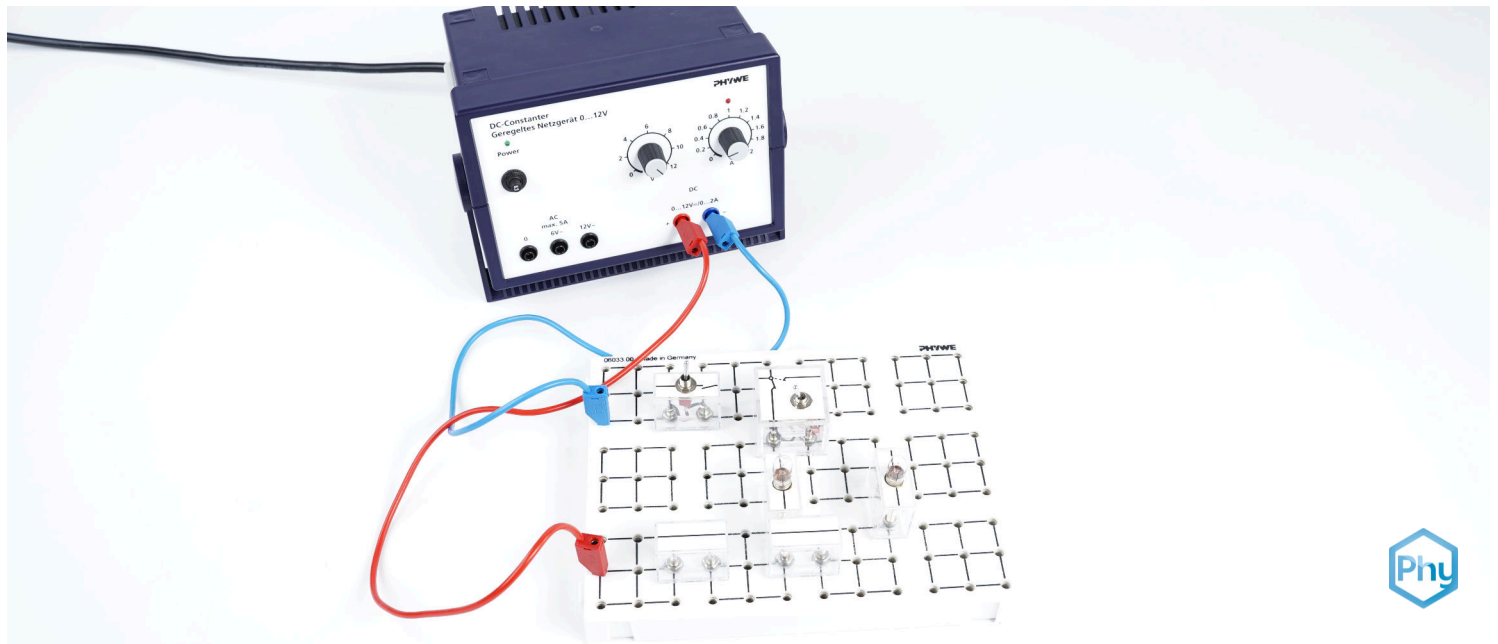


# Changeover switches and alternating switches



Physics

Electricity &amp; Magnetism

Simple circuits, resistors &amp; capacitors



Difficulty level

easy



Group size

2



Preparation time

10 minutes



Execution time

20 minutes

This content can also be found online at:



<https://www.curriculab.de/c/6877636748347a000292b86a>


PHYWE

## Teacher information



## Application

PHYWE

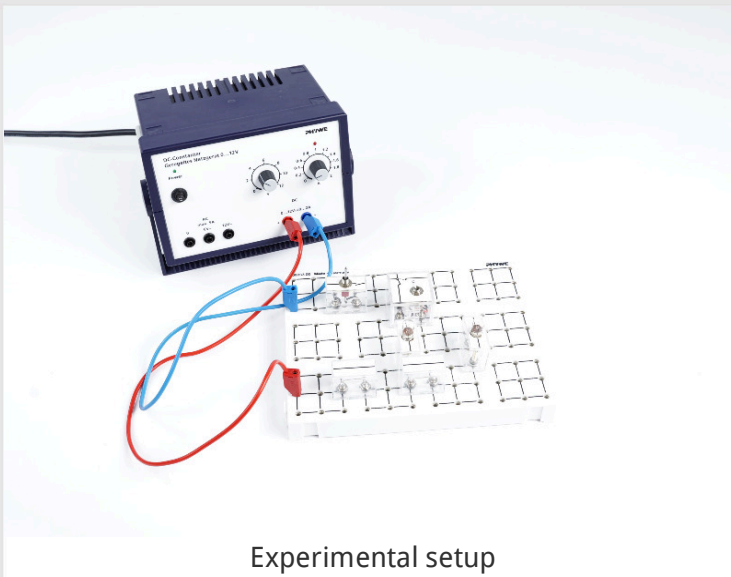

Experimental setup

Switches are very important in electrical engineering because they allow us to intervene manually in a circuit without endangering ourselves. Two relevant types of switches that are frequently used are the changeover switch and the alternating switch.

In this experiment, students will learn how to use these two switches so that they can apply this knowledge independently in the future.

## Other teacher information (1/2)

PHYWE

### Prior knowledge



The students should be able to construct an electric circuit with the help of a circuit diagram and photos.

### Principle



A branched circuit consisting of two simple circuits is set up. The path the current takes—and thus which of the two light bulbs lights up—depends on the position of the changeover switches. This allows pupils to explore independently how the switches must be set to guide the current along the desired path.

## Other teacher information (2/2)

PHYWE

### Learning objective



Pupils should learn how the changeover switches work and develop safe handling skills.

### Tasks



The experiment is divided into two parts. In both parts, the circuit should first be set up according to the sketches and then the behaviour of the light bulbs for the different switch positions should be observed.

## Safety instructions


PHYWE



The general instructions for safe experimentation in science lessons apply.


PHYWE

## Student information

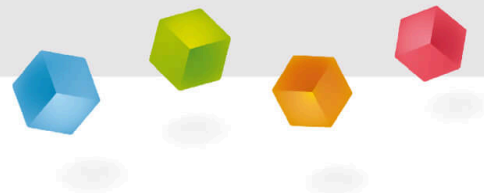

## Motivation

PHYWE

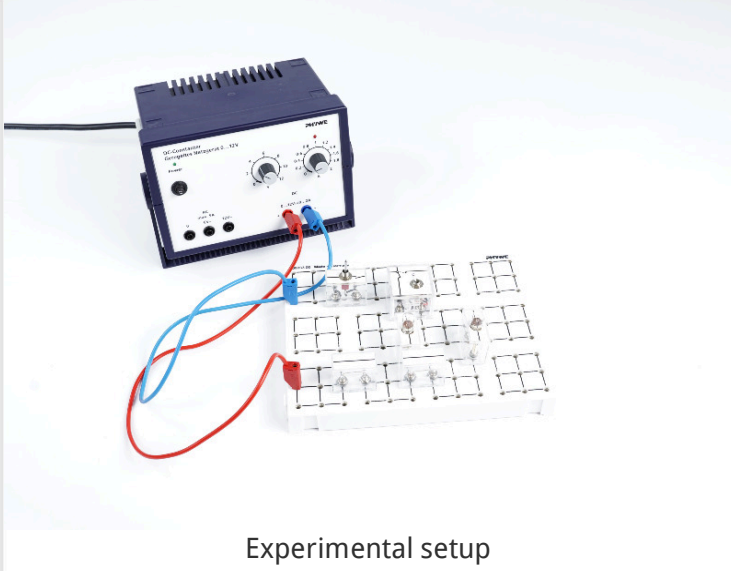

Experimental setup

- Switches are very important in electrical engineering because they allow us to intervene manually in a circuit without endangering ourselves. Two relevant types of switches that are frequently used are the changeover switch and the alternating switch.
- In this experiment, students will learn how to use these two switches so that they can apply this knowledge independently in the future.

## Tasks

PHYWE




1. Set up the first experimental section with the help of a circuit diagram and photos.
2. Note the behaviour of the light bulb for the different switch settings
3. Repeat these two steps for the second experimental setup

## Equipment

Position	Material	Item No.	Quantity
1	<a href="#">Plug-in board, for 4 mm plugs</a>	06033-00	1
2	<a href="#">on-off switch, G1</a>	39139-00	1
3	<a href="#">Change over switch, G3</a>	39169-00	2
4	<a href="#">Wire building block, housing G1</a>	39120-00	3
5	<a href="#">Lampholder E10, case G1</a>	17049-00	2
6	<a href="#">Connecting cord,19 A,25cm, red</a>	07313-01	1
7	<a href="#">Connecting cord,19 A,25cm, blue</a>	07313-04	1
8	<a href="#">Filament lamps 12V/0.1A, E10, 10 pieces</a>	07505-03	1
9	<a href="#">PHYWE Power supply, 230 V,DC: 0...12 V, 2 A / AC: 6 V, 12 V, 5 A</a>	13506-93	1

## Setup I (1/2)

PHYWE

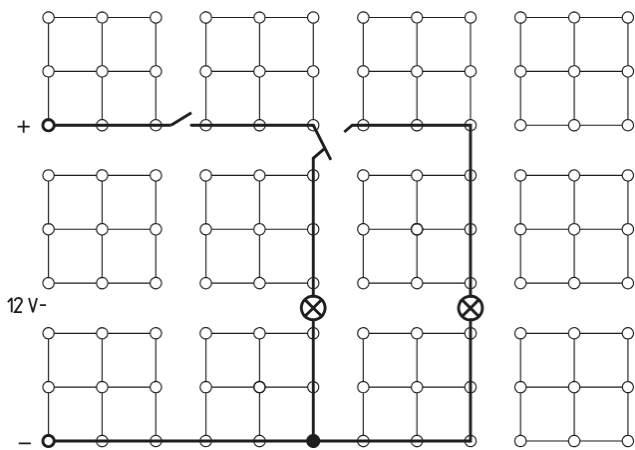


Circuit diagram 1



- Assemble the circuit according to the sketch on the left. You can view a photo of the assembled circuit by pressing the blue button. The switch should be open at the beginning.
- Make sure that the 12 V-bulb is connected. You can recognize it by the fact that this value is engraved on the lamp.

## Setup I (2/2)

PHYWE

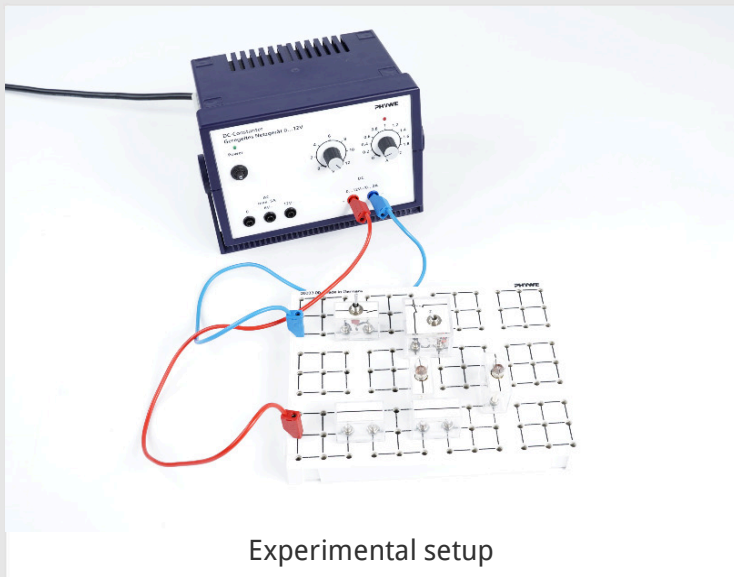


Experimental setup

- Now connect the power supply unit and set it to the voltage of 12 V.

## Procedure I

PHYWE

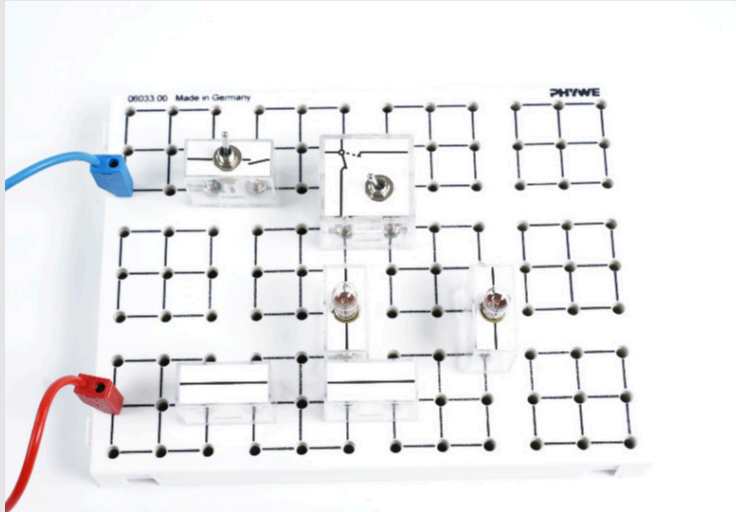


Circuit

- Now close the switch, observe the light bulbs, and record your observations under Observation 1 in the report section.
- While the switch is closed, press the changeover switch several times and record the behaviour of the light bulbs under Observation 2 in the report section.
- Then switch off the power supply unit.

## Setup II

PHYWE

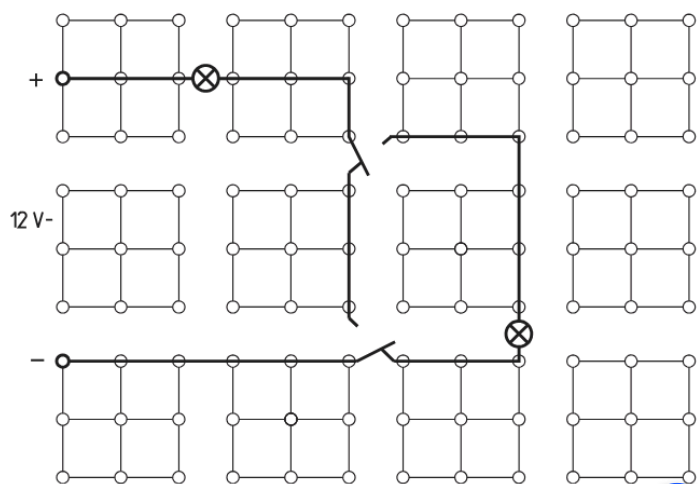


Circuit

- Make sure that the power supply unit is switched off.
- Rebuild the circuit on the breadboard according to the circuit diagram shown on the left. If it helps, you can display a photo of the breadboard by pressing the blue button.
- The circuit you are building here is also called an alternating circuit.



## Procedure II


PHYWE

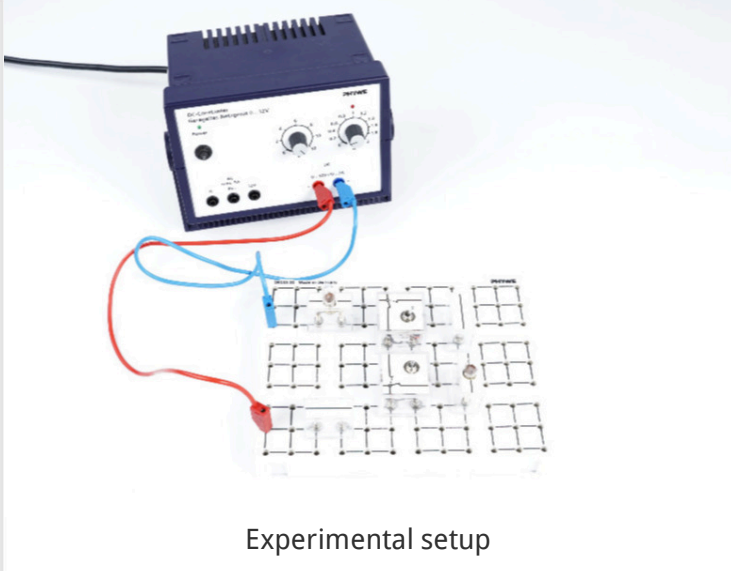

- Switch on the power supply unit and set it to the voltage of 12 V.
- Try different positions of the alternating switches and record your observations under Observation 3 in the report section.
- Then set the power supply unit to 0 V and switch it off.

PHYWE

## Report

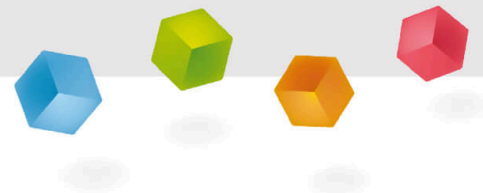

## Observations

PHYWE

Observation 1

Observation 2

Observation 3

## Task 1

PHYWE

Drag the correct words into the gaps

A changeover switch has  connections. One of these can be connected alternately to one of the other two connections by switching. A changeover switch can therefore be used to  from one electrical device to another within a circuit.

In the second part of the experiment, an  was set up. Its advantage is that you can switch an electrical device on and off at . Such a circuit is required for corridor lighting, for example.

series circuit

two

three

two arbitrarily distant locations

switch

alternating circuit

only one location

Slide

Score / Total

Slide 17: Changeover and alternating switches

0/7

Total amount



Solutions



Repeat



Export text