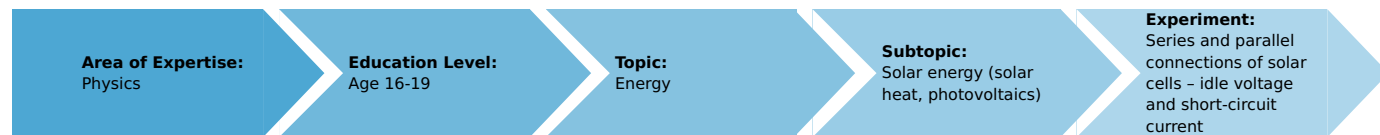


# Series and parallel connections of solar cells - idle voltage and short-circuit current (Item No.: P1382800)

## Curricular Relevance



### Difficulty



Intermediate

### Preparation Time



10 Minutes

### Execution Time



10 Minutes

### Recommended Group Size





2 Students

**Additional Requirements:**
**Experiment Variations:**
**Keywords:**

## Principle and equipment
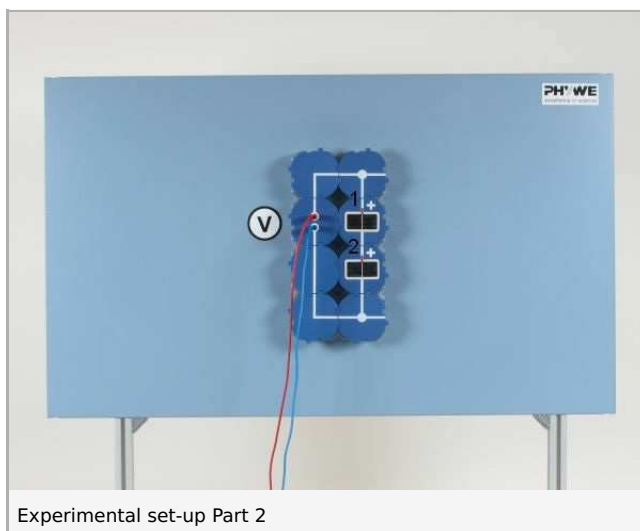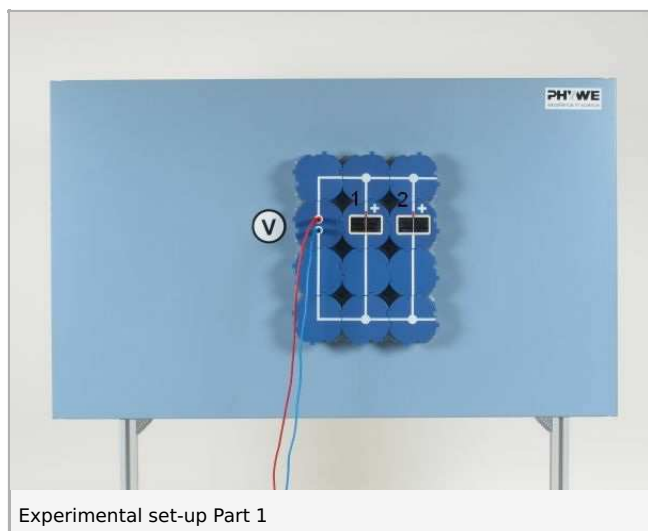
### Principle

The effect of connecting solar cells in series or parallel on their idle voltage and short-circuit current is to be examined.





## Equipment

Position No.	Material	Order No.	Quantity
1	Multimeter ADM2, demo., analogue	13820-01	1
2	Demo Physics board with stand	02150-00	1
3	Ceramic lamp socket E27	06751-01	1
4	Solar cell (2.5x5)cm,module DB	09470-00	2
5	Clamp on holder	02164-00	1
6	Connector interrupted, module DB	09401-04	1
7	Electr.symbols f.demo-board,12pcs	02154-03	1
8	Connector, straight, module DB	09401-01	5
9	Connector, angled, module DB	09401-02	2
10	Connector, T-shaped, module DB	09401-03	4
11	Filament lamp,220V/120W,w.refl.	06759-93	1
12	Support rod, stainless steel, 500 mm	02032-00	1
13	Connecting cord, 32 A, 1000 mm, red	07363-01	1
14	Connecting cord, 32 A, 1000 mm, blue	07363-04	1

## Set-up and procedure
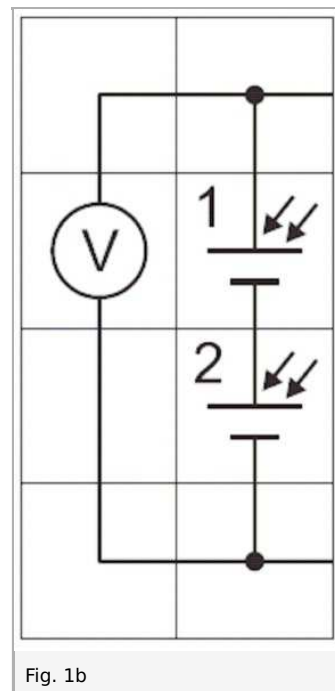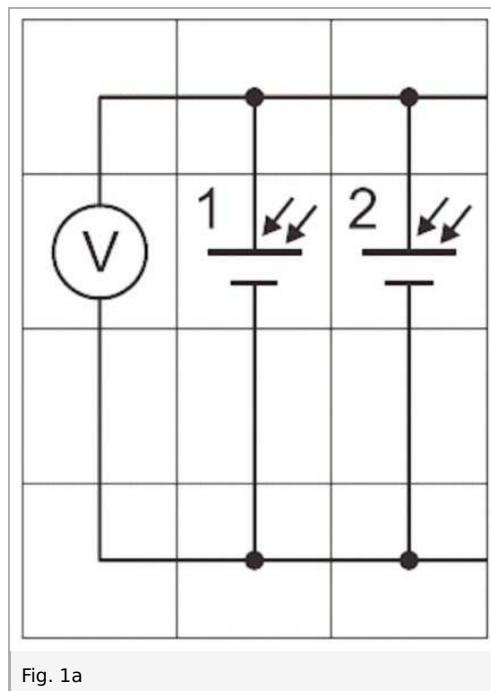
### 1. Measurement of the idle voltage

- Connect up the circuit as in Fig. 1a; use the support material and the clamp to attach the reflector lamp to the top edge of the board in a position that will allow it to irradiate each of the solar cells with the same illuminating intensity.
- Select the 3 V- measurement range, switch on the lamp; insert solar cell 1 in the circuit, measure the idle voltage  $U_0$ , enter the measured value in Table 1.
- Replace solar cell 1 by solar cell 2, measure and note the idle voltage.
- With both solar cells in the circuit, measure and note the idle voltage.
- Change the circuit to that shown in Fig. 1b, first replace solar cell 2 by a straight connector module, measure and note the idle voltage.
- Replace solar cell 1 by solar cell 2, measure and note the idle voltage.
- With both solar cells in the circuit, measure and note the idle voltage, switch off the lamp.



### 2. Measurement of the short-circuit current

- Change the circuit to that shown in Fig. 2a; select the 300 mA- measurement range, switch on the lamp and successively insert one solar cell, the other solar cell, then both of them, illuminate them as uniformly as possible and note the measured values for the short-circuit current  $I_{SC}$ .
- Change the circuit to that shown in Fig. 2b; first successively replace solar cell 1 and solar cell 2 by a straight connector module, then illuminate both solar cells as uniformly as possible; measure the short-circuit current  $I_{SC}$  and note the measured values.

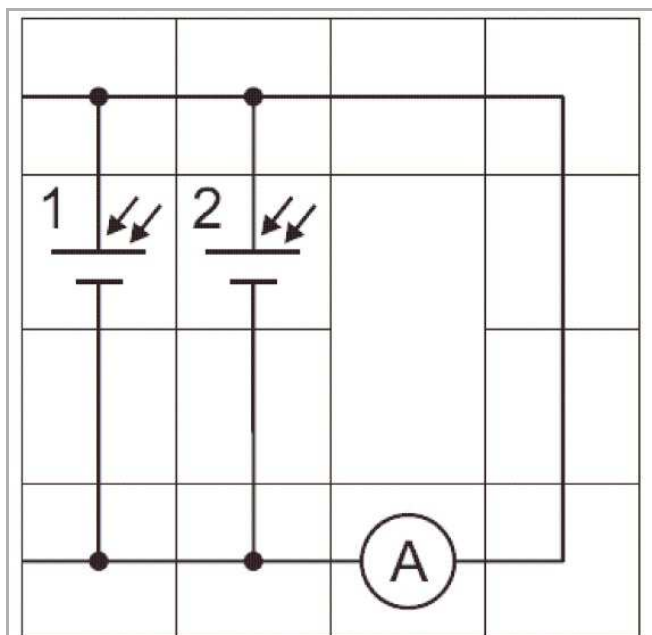


Fig. 2a

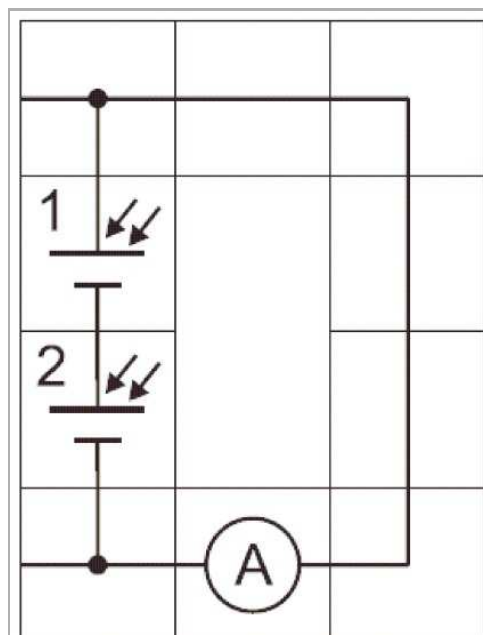


Fig. 2b

## Observation and evaluation

### Observation

Table 1

Connection	Solar cell	$\frac{U_0}{V}$	$\frac{I_K}{mA}$
In parallel	1	0.53	150
	2	0.52	140
	1 and 2	0.53	290
In series	1	0.51	145
	2	0.51	150
	1 and 2	1.05	145

### Evaluation

With a parallel connection of two solar cells no increase in the idle voltage is attained. The short-circuit currents of the two solar cells are additive to each other, however, so that the short-circuit current reaches about the doubled value in the parallel connection.

With a series connection of two solar cells the idle voltages are additive, so that two solar cells connected in series give an idle voltage that is double the value for a single solar cell. An increase in the short-circuit current cannot be attained by connecting two solar cells in series.

### Remarks

When one of two illuminated solar cells in a parallel connection is covered by a hand or piece of paper, the shortcircuit current is reduced to the value for one solar cell, whereas the idle voltage remains almost constant.

In a series circuit, covering one solar cell leads to a large reduction in the short-circuit current, as the high resistance of the solar cell that is no longer illuminated influences the current. This makes the demand for uniform illumination, particularly in a series connection of several solar cells, understandable. In practice, solar modules are used which have a number of solar cells connected in parallel and in series, so that here also uniform illumination must be strived for.