

Current transformation (DEMO)



Physics

Electricity & Magnetism

Electromagnetism & Induction

Physics

Electricity & Magnetism

Use of electrical energy, energy supply



Difficulty level

medium



Group size

-



Preparation time

10 minutes



Execution time

20 minutes

This content can also be found online at:



<http://localhost:1337/c/6478fa50e6e35e00020403a7>

PHYWE

Teacher information



Application

PHYWE



Experimental setup

Transformers are needed to transform input currents higher, lower or equal. Current transformers are usually built into the power supply unit of many electrical devices. In this experiment, the dependence of the number of turns and the current strength is investigated.

If a transformer is heavily loaded on the secondary side, the current strength in the secondary circuit depends on the primary current strength and the number of turns of the coils.

To investigate the regularity, different transformers are examined, first keeping the number of turns and current constant on the primary side and then on the secondary side.

Other teacher information (1/2)

PHYWE

Prior knowledge



No prior knowledge is required.

Principle



When alternating current flows through a coil, it creates a varying magnetic field, which in turn can induce a current in another coil.

In contrast to the voltages, the currents in a transformer are inversely proportional to the windings. Furthermore, if the primary current flows in a counterclockwise direction through the coil, the current in the secondary coil flows in exactly the opposite direction. By applying the flow theorem, the following applies:

$$I_1 \cdot n_1 = I_2 \cdot n_2$$

Other teacher information (2/2)

PHYWE

Learning objective




Students should understand how alternating currents can be converted into lower and higher currents.

Tasks



Investigate the relationship between the number of turns and the currents.

PHYWE

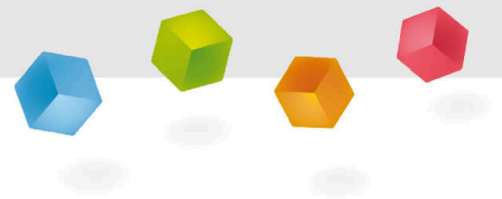

Student information

Motivation

PHYWE

Transformers are built into many electrical devices. In order to transform current well, the coils must not be too far apart and an iron core is important.

This experiment investigates the relationship between current strength and number of turns.



Transformer station

Equipment

Position	Material	Item No.	Quantity
1	PHYWE Variable transformer with digital display DC: 0...20 V, 12 A / AC: 0...25 V, 12 A	13542-93	1
2	PHYWE Demo Multimeter ADM 3: current, voltage, resistance, temperature	13840-00	2
3	Iron core, U-shaped, laminated	06501-00	1
4	Iron core, I-shaped, laminated	06500-00	1
5	Pins for iron cores, U-shaped	06502-00	1
6	Clamping device for iron cores	06506-00	1
7	Coil, 300 turns	06513-01	2
8	Coil, 600 turns	06514-01	1
9	Coil, 1200 turns	06515-01	1
10	Connecting cord, 32 A, 750 mm, black	07362-05	3
11	Connecting cord, 32 A, 750 mm, blue	07362-04	2

Set-up

PHYWE

Set up the experiment according to Fig. 1.

- Place two coils with 300 turns on the U-core.
- Insert the iron pins into the legs of the U-core and put on the yoke.
- Press the transformer firmly together using the clamping device.
- Connect the primary coil to the AC output of the regulating transformer via a measuring device. Select the measuring range 1 A~.
- Connect the secondary coil to the second meter. Select the measuring range 1 A~.



Fig. 1

Procedure (1/2)

PHYWE

Experiment 1

- Adjust the voltage at the regulating transformer so that the primary current is $I_1 = 1\text{A}$.
- Read the secondary current strength I_2 and enter it in Table 1 in the report.
- Change the transformer, insert the secondary coil with 600 turns and repeat the measurement. Choose a suitable measuring range.
- Select the secondary coil with 1200 turns and repeat measurement.


Procedure (2/2)

PHYWE

Experiment 2

- Build the transformer with primary coil and secondary coil of 300 turns each.
- Adjust the voltage at the regulating transformer so that the secondary current strength is $I_2 = 500\text{mA}$.
- Read the primary current I_1 and enter it in Table 2.
- Change the transformer, insert the primary coil with 600 turns and repeat the measurement. Choose a suitable measuring range.
- Select the primary coil with 1200 turns and repeat the measurement.

PHYWE

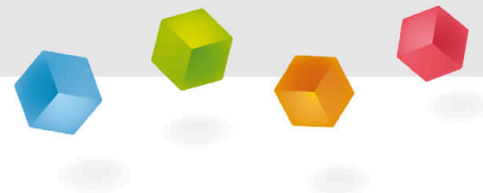

Report

Task (1/5)

PHYWE

Table 1: $n_1 = 300$; $I_1 = 1 \text{ A}$

n_2	$I_2 \text{ [mA]}$	n_1/n_2	I_1/I_2
300	<input type="text"/>	<input type="text"/>	<input type="text"/>
600	<input type="text"/>	<input type="text"/>	<input type="text"/>
1200	<input type="text"/>	<input type="text"/>	<input type="text"/>

Task (2/5)

PHYWE

Table 2: $n_2 = 300$; $I_2 = 500 \text{ mA}$

n_1	$I_1 \text{ [mA]}$	n_1/n_2	I_1/I_2
300	<input type="text"/>	<input type="text"/>	<input type="text"/>
600	<input type="text"/>	<input type="text"/>	<input type="text"/>
1200	<input type="text"/>	<input type="text"/>	<input type="text"/>

Task (3/5)

PHYWE

Drag the words into the correct boxes!

A number of turns of the primary coil n_1 and a constant primary current I_1 causes an in the number of turns n_2 of the secondary coil and a of the secondary current intensity I_2 .

constant

increase

reduction

☒ Check

Task (4/5)

PHYWE

Drag the words into the correct boxes!

Table 1 shows that is roughly halved when the number of turns doubles. With a constant number of turns in the n_2 , a higher number of turns in the n_1 requires a lower I_1 in order to achieve a desired constant I_2 .

primary current

primary coil

current

secondary coil

secondary current

☒ Check

Task (5/5)

PHYWE

Drag the words into the correct boxes!

Table 2 shows that if the n_1 is doubled, the I_1 only has to be about half as large in order to keep the constant.

The following relationship exists between the current strengths and the number of turns on a transformer heavily loaded on the secondary side:

The in the primary and secondary circuits are inversely related to each other like the number of turns.

current strengths

primary current

number of turns

secondary current

 Check

Slide

Score/Total

Slide 14: Transformer summary


0/3

Slide 15: Constant primary current

0/5

Slide 16: Constant secondary current

0/4

Total score  0/12 Show solutions Repeat Export text

10/10