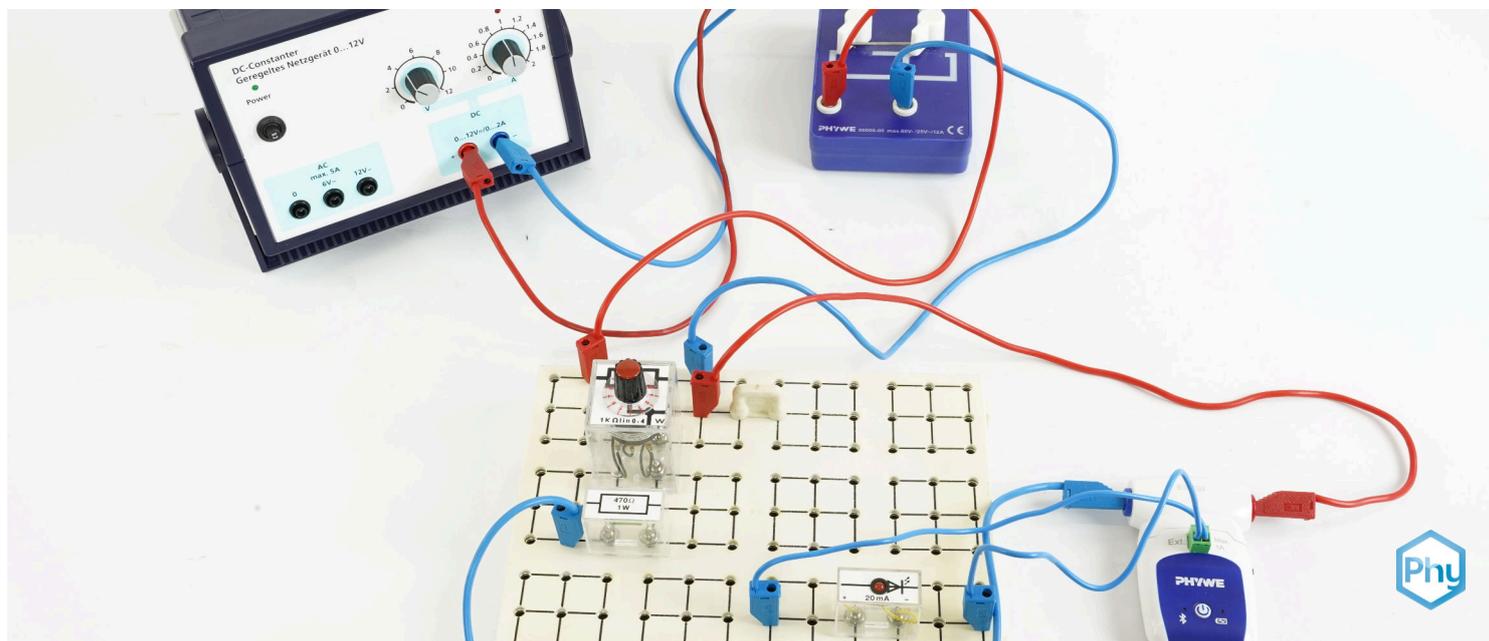


Characteristic curves of semiconductors with Cobra SMARTsense



Physics

Electricity & Magnetism

Electronics



Difficulty level

-



Group size

-



Preparation time

20 minutes



Execution time

20 minutes

This content can also be found online at:



<http://localhost:1337/c/649450a457c3010002623c40>

PHYWE

General information



Application

PHYWE

Semi-conductors are used widely in sensor technology such as cameras and an understanding of them is very important for fields such as solid state physics and particle physics.

This experiment can be used to gain a first understanding of semi-conductors.

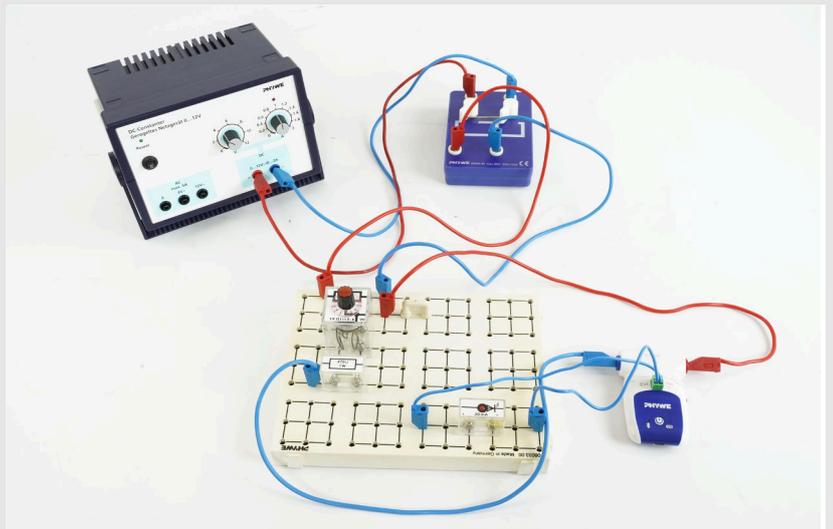


Fig.1: Experimental set-up

Other information (1/2)

PHYWE



Prior

knowledge



Main

principle

The prior knowledge required for this experiment is found in the theory section.

The current-voltage characteristics of different semiconducting diodes is measured. For a npn-transistor the collector current in dependence on the collector-emitter voltage is measured for different values of base current strength. The collector current is measured in dependence on base current. The base voltage is observed in dependence on base current.

Other information (2/2)

PHYWE



**Learning
objective**



Tasks

The goal of this experiment is to investigate the characteristics of semi-conductors.

Measure the current – voltage curve for 1N4007 and 1N4148 silicon diodes, a germanium diode, a Zener-diode and a red LED.

Theory (1/12)

PHYWE

p-n junction properties

A p-doped semiconductor contains impurities called acceptors that can catch electrons from the valence band. E.g. in a typical semiconductor made of atoms with four valence electrons like silicon this might be an element of group III in the periodic table, e.g. boron. The reacting electron level is near the band edge, so that at room temperature a considerable part of these levels is occupied thus forming holes in the valence band. The holes in the valence band act as mobile charge carriers while the acceptor ions stay immobile in the crystal lattice.

In a similar way an n-doped semiconductor contains impurities called donors capable of delivering electrons by thermal excitation to the conduction band as mobile carriers. For a four-valent semiconductor of group IV these would be elements of group V such as phosphorous.

In thermal equilibrium the Fermi level usually lies in between the band edge and the ionized impurity levels.

Theory (2/12)

PHYWE

When an n-doped and a p-doped semiconductor are brought in contact, a p-n junction forms:

In the contact area some electrons from the donors of the n-doped semiconductor recombine with the acceptors of the p-doped semiconductor without creating mobile charge carriers but creating a space charge, a barrier layer. The electric field of this space charge equalizes the Fermi levels of both parts and affects the mobility of charge carriers in the valence- or conduction band. In both of them the space charge is such that it repels the mobile carriers. So the contact area is depleted of carriers – a depletion zone is formed (Fig. 2).

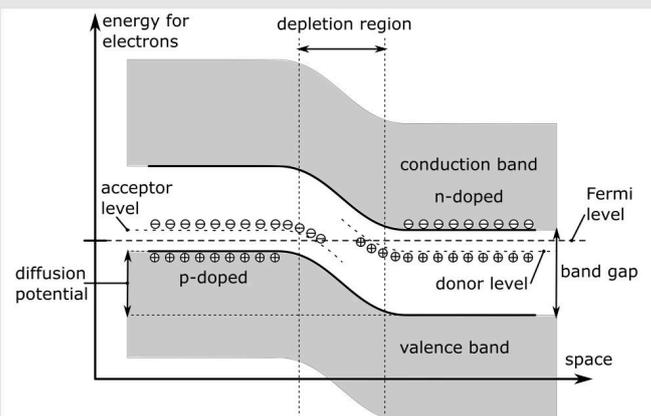


Fig. 2: p-n junction with equally strong impurity concentrations on both sides without external electric biasing field

Theory (3/12)

PHYWE

A p-n junction almost completely blocks electric conduction. Since the activation energies of these reactions are within thermal energy range at room temperature, there is a diffusion current inside the depletion layer - impurities keep releasing and catching charges from their surrounding impurity levels or energy bands. A smaller fraction on the surface of the space charge region can also release their charges to the outside of the space charge region producing a reverse current, if there is reverse bias on the junction, or a forward current for small forward bias.

If a voltage is applied to such a device the polarity makes a difference: If the negative terminal is connected to the p-doped part, this is called reverse biasing of the diode. The energy level of the electrons is raised in the p-doped and lowered in the n-doped section.

Theory (4/12)

PHYWE

The space charge can increase now because it is for more impurities energetically favorable to recombine with the other impurity type until the field inside the bulk p- or n-doped section vanishes again - remember it is electrically conducting. So the depletion layer gets thicker and the space charge electrical field stronger. The p-n junction still blocks electrical conduction as the mobile carriers are repelled from the space charge region.

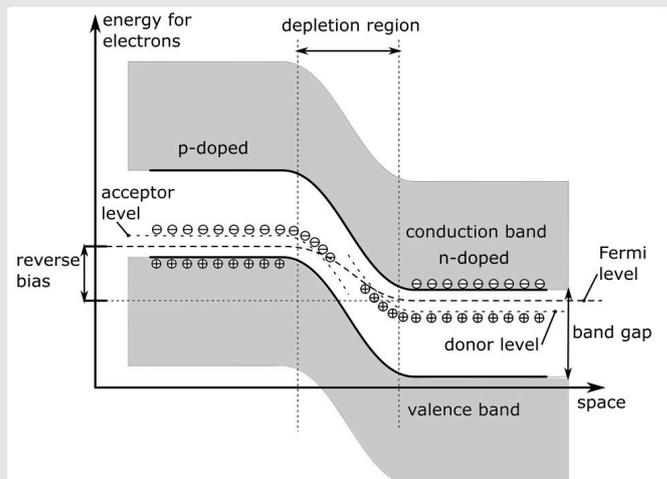


Fig. 3: p-n junction with reverse bias

Theory (5/12)

PHYWE

Forward biasing the diode means to put the positive terminal to the p-doped part. Then, at low voltages, still no current flows since the carriers would have to get over the diffusion potential to cross the depletion layer. Only if the voltage equals the diffusion potential, the band edges “get straight”, the space charge and the depletion layer get dissolved and forward current can flow. Holes and electrons can enter the oppositely doped region and recombine there.

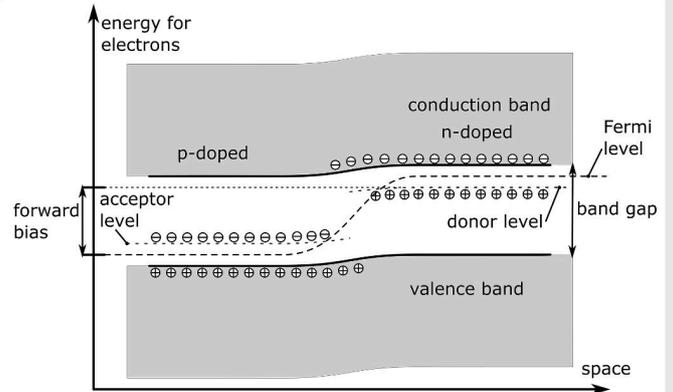


Fig. 4: p-n junction with forward bias

Theory (6/12)

PHYWE

Shockley ideal diode equation

$$I = I_S \left(e^{\frac{V_D}{n k_B T / e}} - 1 \right)$$

with diode current I , reverse saturation current I_S , quality factor n , Boltzmann constant k_B , temperature T and electron charge e .

If ohmic resistance is negligible and the current large compared to reverse current, then this equation predicts an exponential increase of the current with the voltage. So an ideal diode can be used in combination with a linear operational amplifier for a circuit that outputs the logarithm of an input signal or the inverse of that. Adding voltages can be done with resistors, so two of those circuits can perform a multiplication of input signals. Thus diodes can prove helpful for analogue signal manipulation circuits.

Theory (7/12)

PHYWE

Technical significance

Semiconductor diodes are made of p-n junctions. One main purpose is their operation as electronic valves, allowing conduction in mainly one direction, e.g. as rectifiers. The different properties of the semiconductors cause the different properties of the diodes, that is impurity concentration on both sides, band gap, and if the semiconductor is a direct or indirect one. In direct semiconductors the lower edge of valence band, that is where the minimum energy states are in momentum (k-)space, is at the same momentum where the valence band energy has its maximum. In indirect semiconductors conduction-band energy minimum is not at the same momentum (k-)space position where valence band energy maximum is. So a phonon could serve to supply the needed momentum difference for band-band transitions, changing probabilities for photon reactions, as photon and phonon would have to react simultaneously.

Theory (8/12)

PHYWE

Figs. 2 to 4 do not show the momentum space structure that the bands have - momentum space is inverted usual space for the electrons inside a periodic potential of a crystal.

If the dopant concentration is larger, then the thickness of the depletion layer gets smaller, the electrical fields inside the junction stronger. This can have two consequences: For large dopant concentration the thickness can be small enough that electrons can tunnel through the depletion layer leading to a reverse tunnel current called Zener current. If the doping is strong enough that this can already happen at zero applied voltage, the device is called a tunnel diode. Tunnel diodes have larger reverse than forward conductivity and their curvature of the characteristic curve can be larger than with usual diodes, so they can be HF small signal rectifiers. If the tunnel current is significant for small reverse bias, the device is a Zener diode. As second consequence with lesser dopant concentration there will be a threshold for the electrical field where electrons inside the barrier layer will be accelerated sufficiently that they can by collision excite more electrons into conduction band.

Theory (9/12)

PHYWE

This would be an avalanche breakdown. If the dopant concentration is still high enough that the avalanches don't get destructively large, then the device will also work the same way as a Zener diode. Because most times avalanche and Zener currents are both present, devices are called Z-diodes.

Z-diodes can be used as overvoltage protectors or as voltage regulators as they can branch away current if the voltage is exceeding the rated Z-voltage. For this purpose they are connected in reverse mode.

While tunnel current will increase with rising temperature as the number of participating carriers increases - the temperature coefficient of the Zener voltage is negative but not very dependent on Zener voltage value-, avalanche current will decrease with rising temperature as more carriers will get scattered inside the barrier layer before they can create avalanches - the Z-voltage temperature coefficient is positive, the more, the thicker the barrier layer is that is the higher the Z-voltage is rated. If temperature coefficients of avalanche and Zener current cancel, the devices can be voltage reference diodes.

Theory (10/12)

PHYWE

In case of direct semiconductors – not silicon – the charge carriers of forward current at recombination can emit their energy difference not only thermally but also as photon – useful for LEDs.

The other way around photons can be absorbed inside the semiconductor and excite electrons into conduction band. With presence of a barrier layer the semiconductor can thus work as photodetector or photovoltaic element.

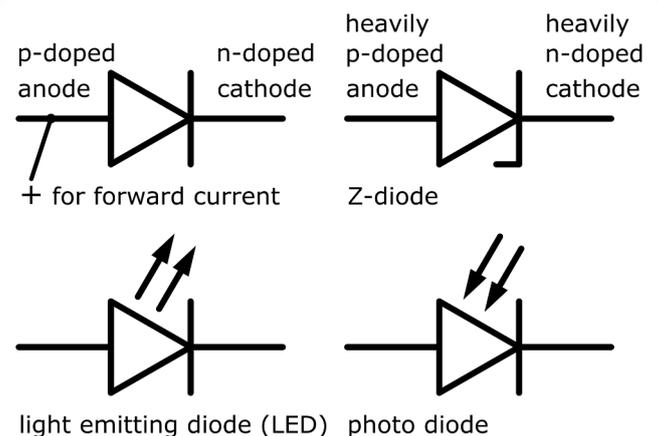


Fig. 5: Diode electronic symbols

Theory (11/12)

A transistor that is formed by two opposite p-n junctions, a pnp or a npn device, is called a bipolar junction transistor. Such a device will block current in either direction – one of the barrier layers will always be reverse biased -, unless carriers are injected in the middle region destroying one of the depletion zones or barrier layers which makes the device permeable to current. So the middle region is electrically contacted and this contact is called base.

To make such a device a good amplifier, the other regions are asymmetrically doped and also of asymmetrical geometry and thus making one contact the emitter and the other the collector.

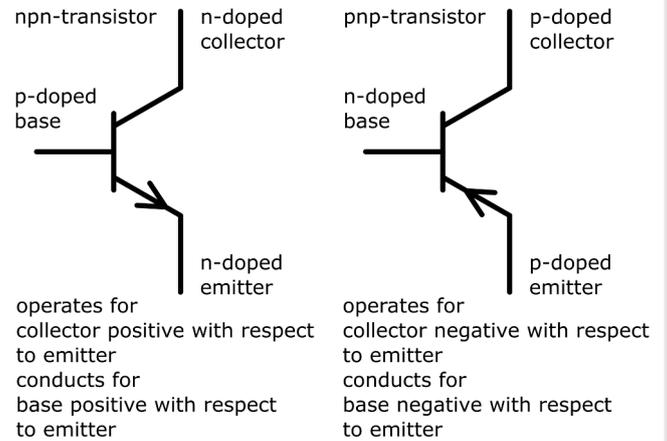


Fig. 6: Bipolar junction transistor electric circuit symbol and function

Theory (12/12)

E.g. with a npn transistor like the BC337 there is only current gain, if the emitter is connected to the negative terminal, the collector to the positive terminal and the base is made a little positive injecting holes into the barrier layer between base and collector and thus weakening it.

Fig. 7 shows the designators usually chosen in data sheets referring to bipolar junction transistor (BJT). The voltage designators U_{XY} denominate the difference: potential at X minus potential at Y. So in datasheets for pnp transistors the entries often read U_{EC} and then contain positive values.

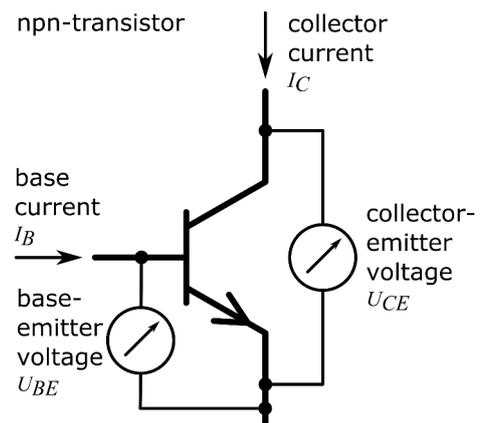


Fig. 7: BJT definitions

Equipment

Position	Material	Item No.	Quantity
1	Cobra SMARTsense Energy - Sensor for measuring electrical current and voltage $\pm 30V / \pm 1A$ (Bluetooth + USB)	12919-00	1
2	USB charger for Cobra SMARTsense and Cobra4	07938-99	1
3	PHYWE Power supply, 230 V, DC: 0...12 V, 2 A / AC: 6 V, 12 V, 5 A	13506-93	1
4	measureLAB, multi-user license	14580-61	1
5	Plug-in board, for 4 mm plugs	06033-00	1
6	bridge plug	06027-07	4
7	Commutator switch	06006-00	1
8	Potentiometer 1 kOhm, 0.4W, G2	39103-04	2
9	Resistor 470 Ohm, 1W, G1	39104-15	1
10	Resistor 1 kOhm, 1W, G1	39104-19	1
11	Resistor 100 Ohm, 1W, G1	39104-63	1
12	Resistor 22 kOHM, 1W, G1	39104-34	1
13	Semiconductor diode Ge, AA118, case G1	39106-01	1
14	Semiconductor diode Si, 1 N 4007, case G1	39106-02	1
15	Semiconductor diode Si, 1 N 4148, case G1	39106-03	1
16	Low power zener diode ZF 4,7, G1	39132-01	1
17	Light emitting diode, red, case G1	39154-50	1
18	Transistor BC337, base left, G3	39127-20	1
19	Connecting cord, 32 A, 500 mm, red	07361-01	4
20	Connecting cord, 32 A, 500 mm, blue	07361-04	4
21	Connecting cord, 32 A, 500 mm, yellow	07361-02	2
22	Connecting cord, 32 A, 500 mm, black	07361-05	2

PHYWE


Setup and Procedure



Setup (1/3)

PHYWE

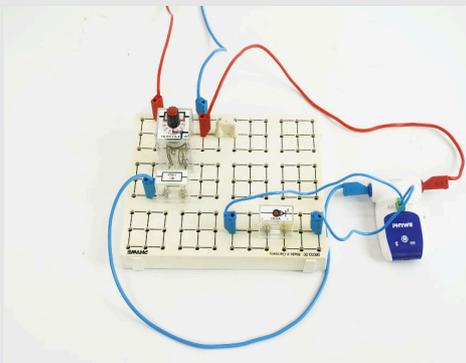The Cobra SMARTsense Energy sensor and measureLab are required to carry out the experiment.



Setup (2/3)

PHYWE

Characteristic curves of diodes

- Connect the power supply to the cross-over switch. The cross-over switch feeds a 1 k Ω potentiometer that then provides on its slider connector a range of -5...5 V if unloaded. Next a 470 Ω resistor limits the maximum current to 10.6 mA maximum which can't destroy any of the diodes. If the diode can pass 10.6 mA at a given voltage, the voltage range on the diode will end there because the rest of the voltage will drop across the 470 Ω resistor and the potentiometer resistance.
- Connect the Cobra SMARTsense Energy sensor as it is shown in the picture, to determine current I and voltage U .

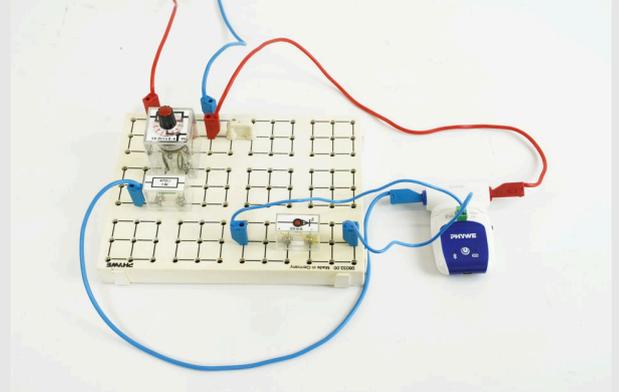


Fig. 8: Circuit for supplying diode voltage and limiting diode current

Setup (3/3)

PHYWE

Set the following settings: Click on the upper left corner of the window the Cobra SMARTsense Energy Icon, click the "Lock" icon if it is open, wait for the red line to turn green, select "Current CH1 I1", select "Digital display", drag "Voltage CH3 U1" into that display. Select "Current CH1 I1", select "Diagram", drag "Voltage CH3 U1" into that diagram, in the diagram click the "diagram" icon, in the drop-down menu "X:" select "Voltage CH3" as x-axis. Now the diagram is ready to display characteristic curves current over voltage.

Now open the settings menu using the gearwheel icon. In "Sensors/Channels" select for CH1: 10 mA, averaging over 50 -100 values; CH3: 10 V, averaging over 50 -100 values. For each Channel select an appropriate number of digits in "Decimal places" and confirm all settings with the "Apply" button in order to transfer settings to the Energy sensor.

In "Measurements" select 100 Hz.

Procedure (1/3)

Procedure: characteristic curves of diodes

Set the control on the potentiometer such that the voltage on the circuit is maximum, that is the potentiometer slider is all the way to the red terminal. Start data recording with the "Start" button in the lower left corner of the measureLAB window. Slowly turn the control so the slider moves towards the blue terminal to the end, then switch the cross-over switch, slowly turn the control all the way back and stop the measurement.

Exchange the diode with the next type and repeat that procedure with all five types of diodes. You should receive a set of characteristic curves that should look like this:

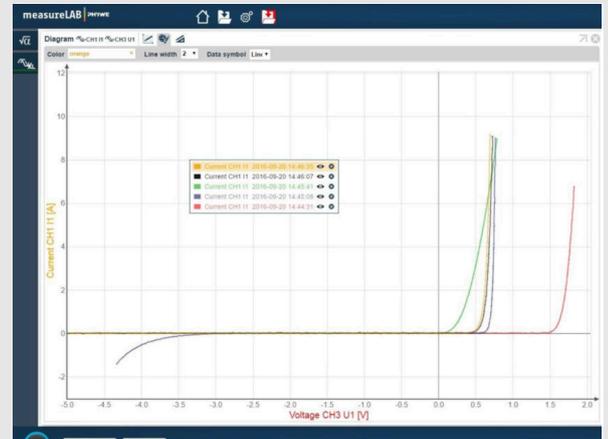


Fig. 9: Example for diode characteristics results

Procedure (2/3)

Fig. 9 shows: Red: Z-diode 4.7, green: Ge-diode AA118, black: Si small signal diode 1N4148, orange: Si rectifier diode 1N4007.

Shockley ideal diode equation

Remeasure the positive branch of the characteristic curves for a LED, Si- and GE-diode. In the diagram window click the diagram icon and set "Y:" to "Log" so you have a logarithmic plot of the current over voltage. If the current would rise exponentially with the voltage, this diagram then would show a linear rise. The result might look like Fig. 10.



Fig. 10: Logarithmic plot of diode current over diode voltage

Procedure (3/3)

PHYWE

From left to right Fig. 10 shows the logarithmic curves of the Ge-diode, of Si-diodes 1N4007 and 1N4148, and the red LED.

The linear section (where current rises exponentially) for Ge is small, for the Si diodes exceeds the measuring range, and for the LED is relatively small again.

For small diode voltages here current signal noise dominates. With sensitive measuring gear the reverse saturation current could be measured. For large currents the ohmic resistance starts to play a role. In the intermediate range the diffusion current dominates and the Shockley diode equation predicting exponential behaviour applies. With some diodes, before ohmic resistance sets in, there can be a deviation from Shockley law when the current exceeds the diffusion current assumed in this law.

The ohmic resistance of the Ge diode is relatively large, followed by the LED.

PHYWE



Evaluation

Results

PHYWE

The measured characteristic curves show that for the measured diodes the current is only on for one polarity of the voltage except for the Z-diode, which can also conduct in reverse direction - but for a larger threshold than in forward direction.

Also it shows that forward voltage depends on the semiconductor material.

Germanium forward voltage is lower than silicon forward voltage. The red LED (GaAsP) has the highest forward voltage.

The logarithmic plot proves that there is a range where the diodes behave according to Shockley ideal diode equation.

The Ge and GaAsP diodes show larger deviations from Shockley ideal diode behaviour, Zener current and avalanche current are not taken into account for the ideal diode equation.