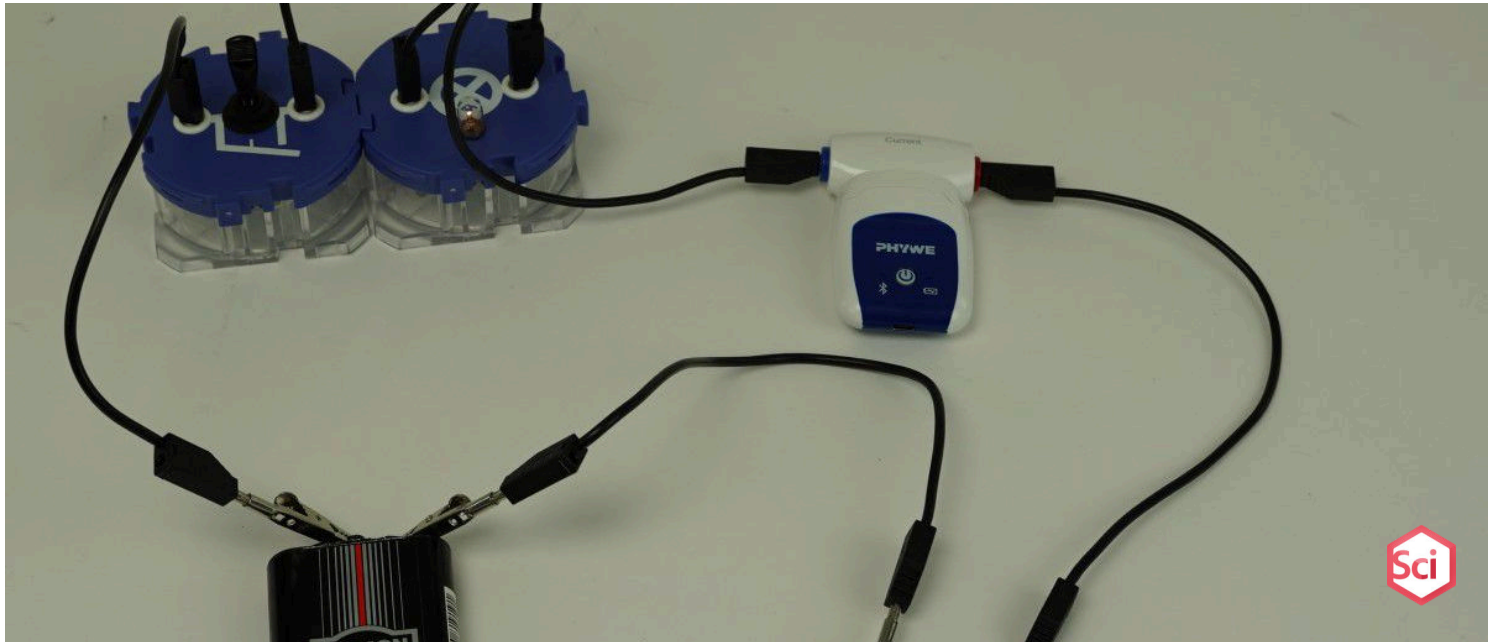


# Conductive and non-conductive materials with Cobra SMARTsense



In this experiment, students learn that different materials have different properties in terms of conductivity.

Nature & technology

Devices & machines in everyday use



Difficulty level

easy



Group size

2



Preparation time

10 minutes



Execution time

20 minutes

This content can also be found online at:



<http://localhost:1337/c/611e02b97f92610003544ed8>


PHYWE

## Teacher information



## Application

PHYWE

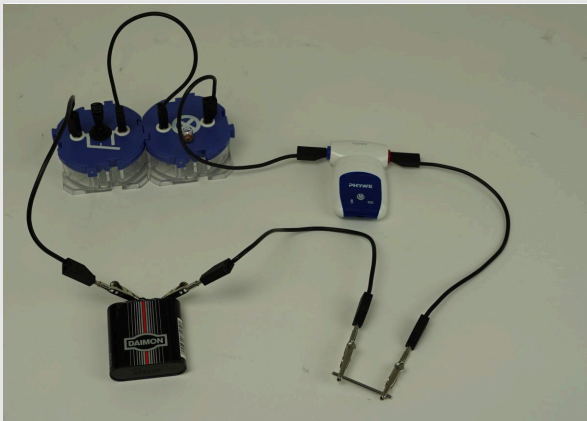

Experiment setup

In this experiment, the students examine the electrical conductivity of various substances. To do this, they use the Cobra SMARTsense Current to observe and record the measurement data in real time. Substances that conduct electricity are called conductors; substances that do not conduct electricity are called non-conductors or insulators.

## Other teacher information (1/3)

PHYWE

### Prior knowledge



Students should already have a good, basic theoretical knowledge of conductive and non-conductive materials.

### Scientific Principle



Various substances are placed into an electric circuit and examined for their conductivity.

## Other teacher information (2/3)

PHYWE

### Learning objective



In this experiment, students learn that different materials have different properties in terms of conductivity.

### Tasks


The students build the circuit and insert different rods. They then insert a beaker into the circuit and fill it with different liquids.

## Other teacher information (3/3)

PHYWE
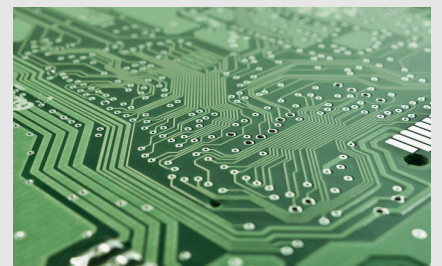
### Application

- Conductors are used to allow the electric current to flow. Non-conductors often enclose them to prevent danger to people.
- The circuit board in a smartphone or computer consists of many electrical lines that are separated from each other by non-conductive layers. This prevents the various circuits from interfering with each other.
- Not only solids, but also liquids or substances dissolved in water can conduct electricity. Substances that do not actually conduct electricity can become conductors when they are wet!



## Safety instructions

PHYWE



- The general instructions for safe experimentation in science lessons to be applied to this experiment.


PHYWE



## Student Information

### Motivation

PHYWE

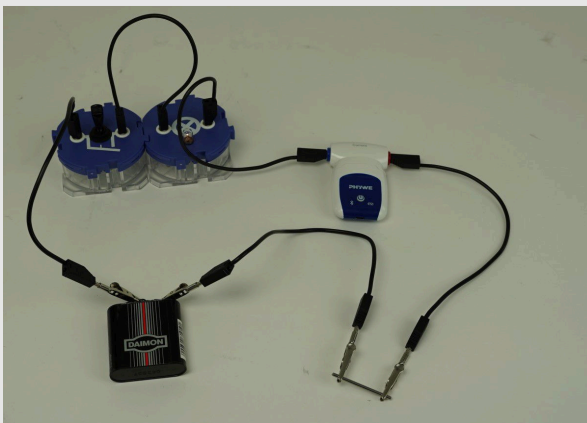

Experiment setup

Perhaps you have already touched an electrically charged pasture fence and received a (painful) electric shock. The electric fence is usually powered by a battery, which is connected to the fence via a power cable.

If you touch this cable, you do not feel an electric shock, although electric current is conducted through the cable as well as through the pasture fence. How can this phenomenon be explained?

## Tasks

PHYWE



In this experiment, you want to investigate the electrical conductivity of different substances and test which ones conduct electricity.


You already know that electric current only flows through a closed circuit. Put different materials into a circuit and observe whether a light bulb in the circuit lights up and whether current flows.

1. Build the circuit and insert different rods.
2. Place a beaker in the circuit and fill it with various liquids.

## Equipment

Position	Material	Item No.	Quantity
1	Flat battery, 4.5 V	07496-01	1
2	Connecting cord, 32 A, 250 mm, black	07360-05	5
3	Alligator clip	167700	4
4	Lamp holder, E10, with sockets	09390-06	1
5	Lamp 4 V/0,04 A, E 10 socket	06154-00	1
6	On/off switch for sciences sets	09390-07	1
7	Conductors/non-conductors, l=50 mm	06107-01	1
8	Beaker, 50 ml, plastic (PP)	46273-01	1
9	Water, distilled 5 l	31246-81	1
10	Sodium chloride 250 g	30155-25	1
11	D (+)-Sucrose 100 g	30210-10	1
12	Spoon, stainless steel, 210 mm	40874-00	1
13	Glass rod, boro 3.3, l=300 mm, d=9 mm	40485-07	1
14	Cobra SMARTsense - Current, $\pm 1$ A (Bluetooth + USB)	12902-01	1

PHYWE

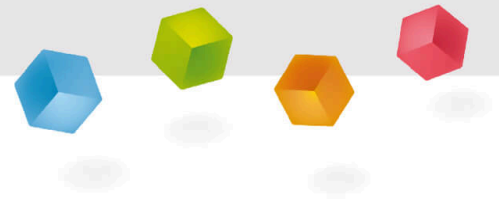

## Structure and procedure

### Structure (1/4)

PHYWE

For measurement with the **Cobra SMARTsense sensors** the **PHYWE measureAPP** is required. The app can be downloaded free of charge from the relevant app store (see below for QR codes). Before starting the app, please check that on your device (smartphone, tablet, desktop PC) **Bluetooth** is **activated**.



iOS



Android




Windows



## Structure (2/4)

PHYWE

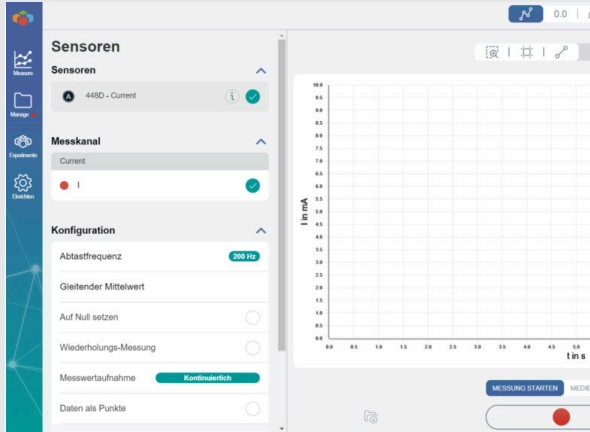


Connected SMARTsense current sensor in the Windows 10 version of measureAPP.

- Turn on the SMARTsense current sensor by pressing and holding the power button.
- Connect the sensor to the device in the measureAPP under the item "Measure".
- The SMARTSense sensor is now displayed in the app.

## Structure (3/4)

PHYWE

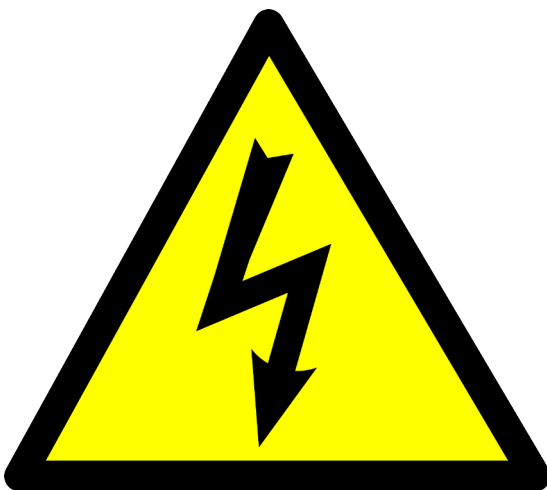

- Make sure that the on/off switch is turned off before connecting the battery. To do this, move the lever up.
- This ensures that no current flows through the circuit. Set the switch only during the measurement and switch it off again afterwards.
- Only change the setup when the on/off switch is turned off!

## Structure (4/4)

PHYWE


Assemble the circuit in the following order:

- Battery - On/Off switch - Lamp holder - SMARTsense current- Conductors and non-conductors (start with a rod of your choice) - Battery

Connect the parts with a cable each.

- You can plug the cables directly into the blue components and the SMARTsense current.
- Clamp an alligator clip to the poles of the battery and the ends of the rods. You can then plug the cable in there.

Put the bulb in the lamp socket.

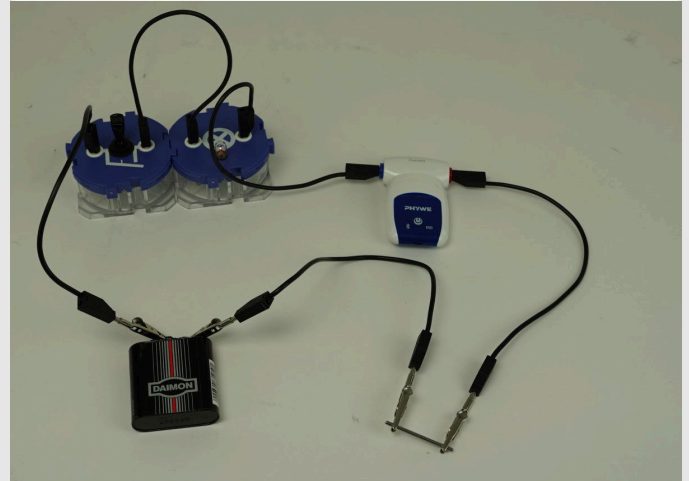

Test setup

## Procedure (1/4)

PHYWE


Press the button "Record" in measureAPP for the measurement.

- Investigate the behavior of the different rods in the "Conductors and Non-Conductors" set. Start with the rod that you inserted into the circuit under "Build".
- Turn on the on/off switch. The circuit is now closed!
- Observe the lightbulb and measure the current with the meter.
- Turn the on/off switch off again!
- Then take the rod out of the circuit and insert the next rod.
- Repeat the measurement for all the rods in the set. Make sure that the switch is always turned off when replacing the rods and record your observations in the table in the results section.
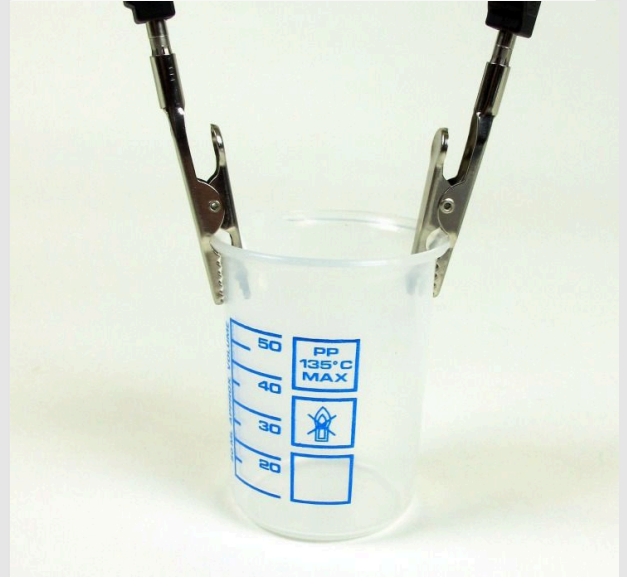
## Procedure (2/4)

PHYWE

- Now take out the last rod. Instead, clamp the cables onto the rim of the cup as shown in the picture on the right.
- Fill the beaker completely with table salt and switch on the on/off switch. The circuit is now closed!
- Observe the bulb and measure the current with the meter.
- Turn the on/off switch off again!
- Remove the table salt completely from the beaker. Repeat the measurement with sugar and then remove the sugar again.



## Procedure (3/4)

PHYWE

- Pour enough distilled water into the beaker until it touches both alligator clips.
  - Turn on the on/off switch. The circuit is now closed!
  - Observe the bulb and measure the current with the meter.
  - Turn the on/off switch off again!
  - Record your observations in the table in the log.
- Add a teaspoon of salt to the cup filled with distilled water. Stir the water with the stirring rod, so that the salt will be dissolved and there is nothing left of it.
  - Turn on the on/off switch. The circuit is now closed!
  - Observe the bulb and measure the current with the meter.
  - Turn the on/off switch off again!

## Procedure (4/4)

PHYWE

- Empty the cup and rinse it out.
- Then fill it again with distilled water and add a teaspoon of sugar. Dissolve the sugar and repeat the measurement.
- Record your observations in your report.



PHYWE

## Report



Task 1

PHYWE

Enter your observations from the experiment in the table.

	Is the light on?	Current (mA)		Is the light on?	Current (mA)
1			6		
2			7		
3			8		
4			9		
5			10		

Task 1

PHYWE

Enter your observations from the experiment in the table.

	Is the light on?	Current (mA)		Is the light on?	Current (mA)
1			6		
2			7		
3			8		
4			9		
5			10		

## Task 2

PHYWE

Does the light goes on when you have one of the sticks plugged into the circuit?

- ☐ No, the lamp never lights up. That's because there is no wire where the stick was clamped into the circuit. Only cables conduct electricity.
- ☐ Yes, the light always goes on when one of the sticks is plugged into the circuit.
- ☐ No, the light doesn't goes always on . For example, if a plastic rod was clamped in the circuit, it remained off.

☒ Check

## Task 3

PHYWE

Compare your results and observations. What did the meter read when the light was on? What does that mean?

## Task 4

PHYWE

You probably already know that metals conduct electricity. Conversely, are all non-metals also non-conductors?

- ☐ No. The salt solution, for example, is not metal, yet it conducted the current and the lamp was on.
- ☐ That's wrong. Only liquids conduct electricity, so you should leave the pool during a thunderstorm.
- ☐ That's right. Only metals can conduct electricity.

☒ Check

## Task 5

PHYWE

In the experiment, you observed the electrical conductivity of salt water and sugar water. What did you notice? Did the observation perhaps even surprise you?

## Task 6

PHYWE

Choose the correct answers.

- ☐ Conductors are allowing the electric current to flow. Non-conductors often enclose them to prevent danger for people.
- ☐ The substances for which the lamp goes on are called insulators.
- ☐ The substances for which the lamp does not light up are called conductors.
- ☐ The substances for which the lamp does not go on are called insulators.

✓ Check